

4.8.2 Electricity Paper 2 (448/2)

EXERCISE 1

- (a) Using the materials and equipment provided, connect the circuit as shown in Figure 1. (3 marks)

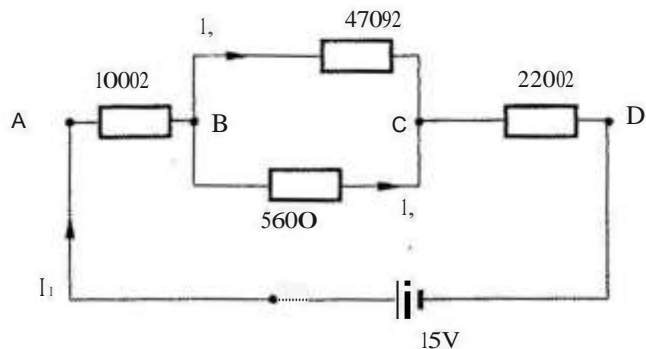


Figure 1

Let the examiner check your work.

- (b) Close switch S, measure and record the values of the following quantities in table 1. (15 marks)

Table 1

	MEASURED VALUES	CALCULATED VALUES
Current: - I_1		26mA
- I_2		14mA
- I_3		12mA
Voltage Drop Across - AB		2.6v
- BC		6.6v
- CD		5.6v

- (c) Give reasons for the differences between the measured values and the calculated values given in the table. (2marks)

EXERCISE 2

Using the tools, materials and equipment provided, fabricate the cell holder shown in figure 2.
(20 marks)


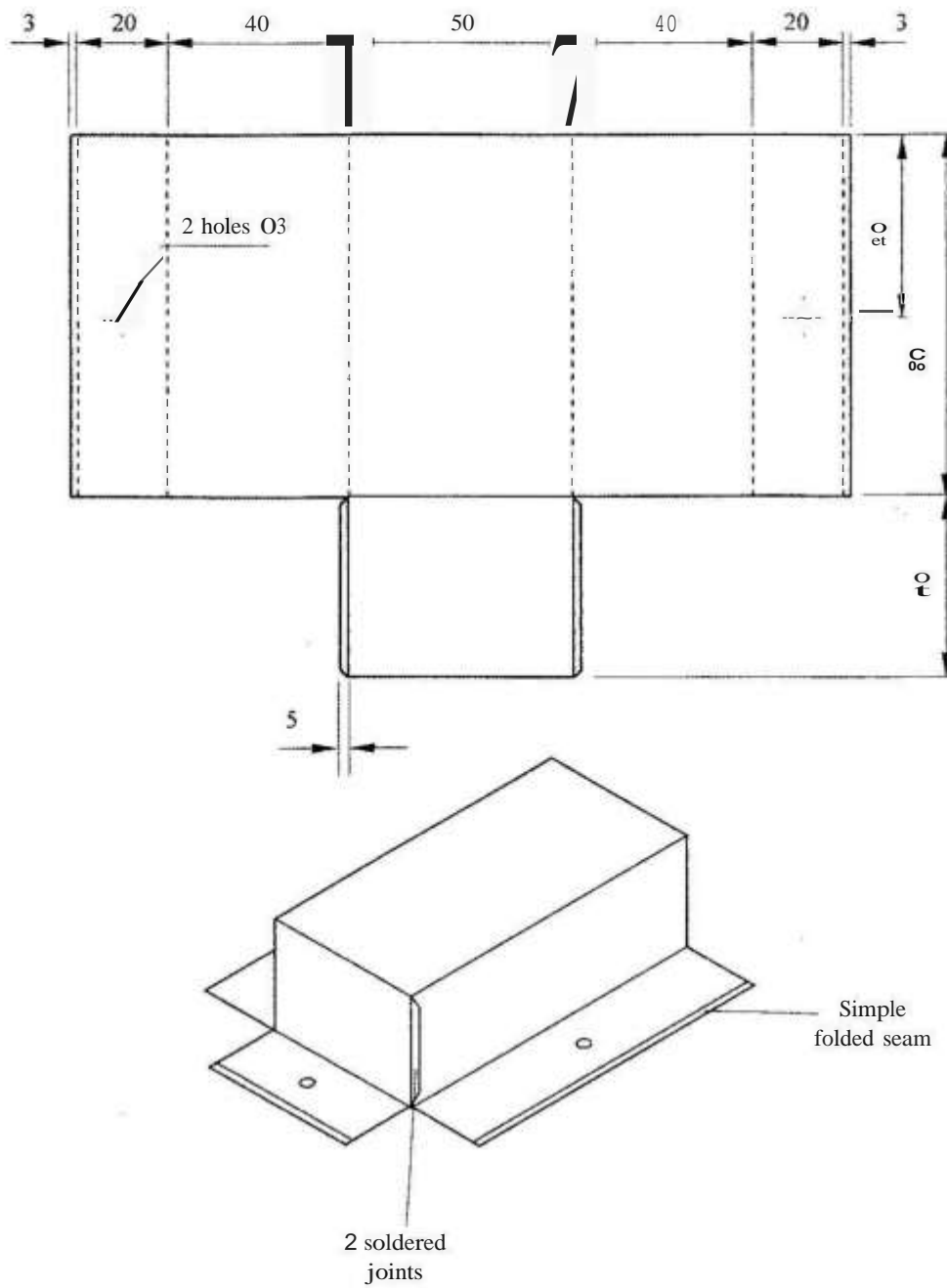


Figure 2

EXERCISE3

Using the tools, materials and equipment provided, carry out the following tasks:

- (a) terminate the three-core flexible cable to the top plug and the iron box. (15 marks)
- (b) turn the thermostat switch to open position. (1 mark)
- (c) measure and record the values of the resistance between:
 - (i) live and neutral at plug
 - (ii) live and earth at plug
 - (iii) earth at plug and at iron box body
 - (iv) neutral at plug and at iron box. (4 marks)
- (d) Draw a graph of current I on horizontal axis against voltage V , on vertical axis. (5 marks)
- (e) From the curve obtained in the graph, state the application of the circuit. (1 mark)
- (9) Name the active device in the circuit. (1 mark)

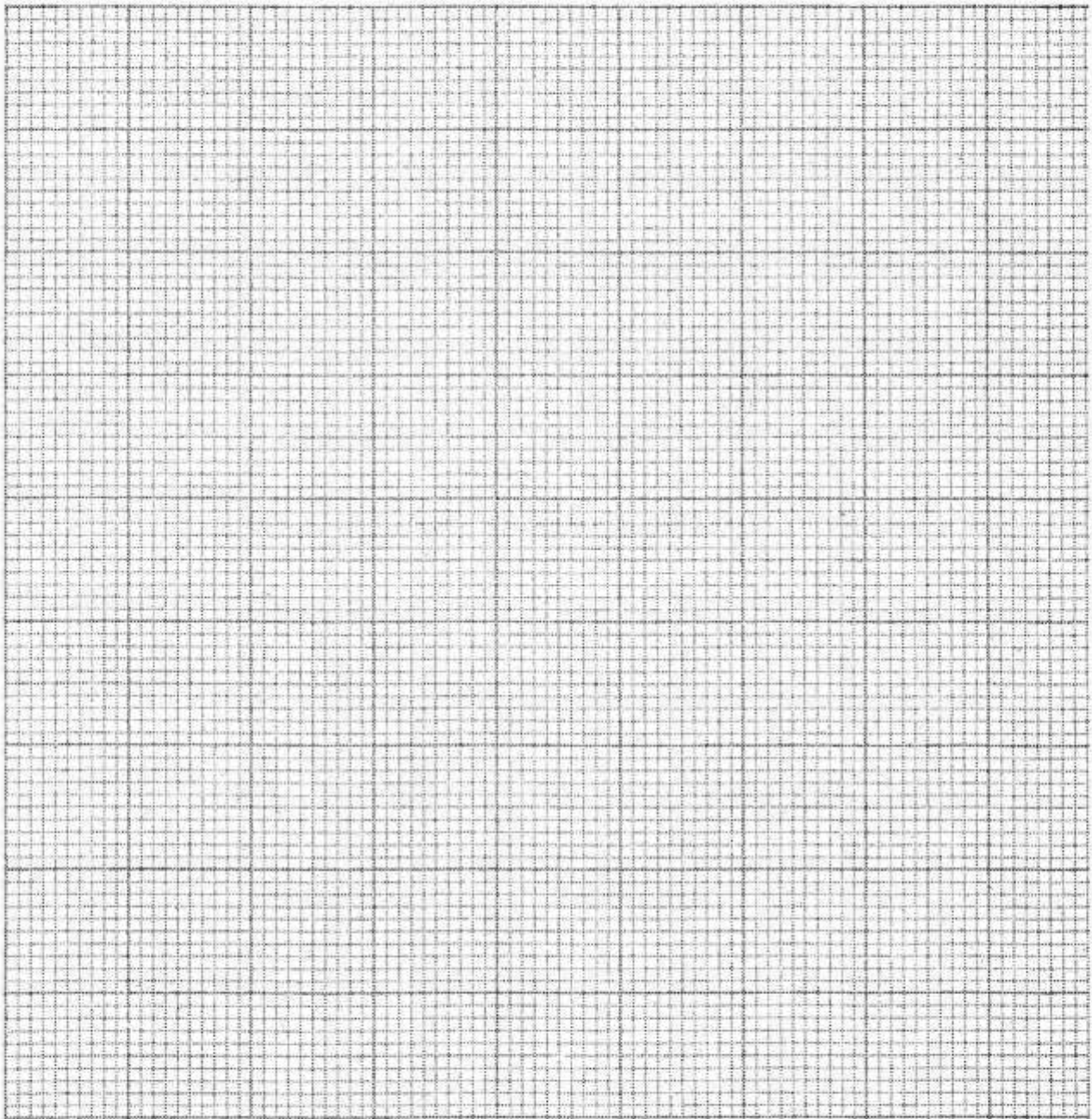

EXERCISE 4

Figure 3 shows the block diagram of a prefabricated circuit Q. Carry out the following tasks.

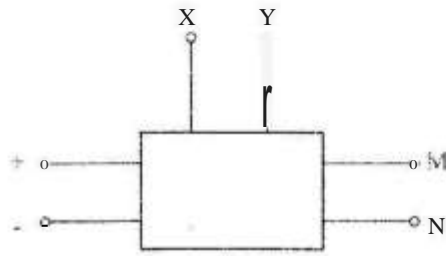


Figure 3

- (a) (i) Adjust the power supply to zero volt.
- (ii) connect the circuit to the power supply through the switch provided. (1 mark)
- (b) Connect (i) the milliammeter provided between points X and Y of the circuit.
- (ii) the voltmeter provided between points M and N of the circuit. (2 marks)
- (c) Close the switch. Adjust the power supply to obtain the voltage values shown in table 2. In each case, measure and record the corresponding values of current I and voltage V_s . (10marks)

Table 2

SUPPLY VOLTAGE V_s	0	2.5	5	6	8
CURRENT I					
VOLTAGE V_x					

EXERCISES

Figure 4 shows the layout of a bell circuit. Using the tools and materials provided, install the circuit such that the two push buttons operate the bell independently.

(20 marks)

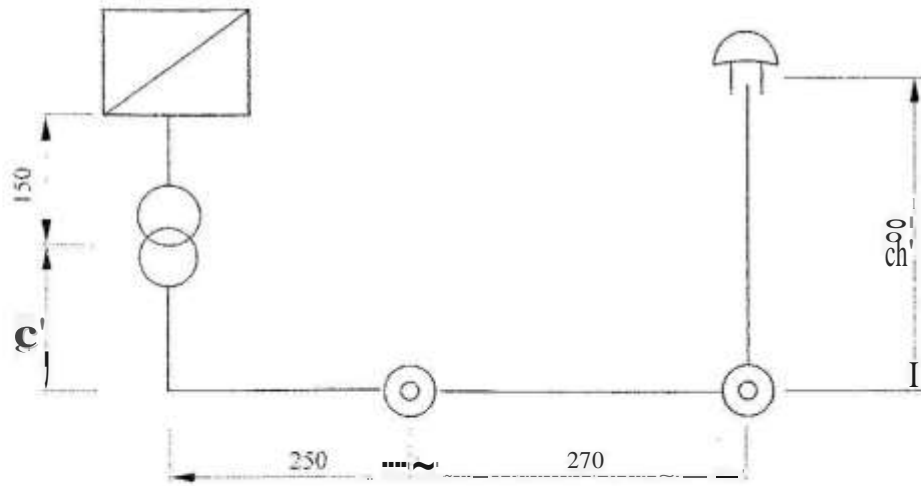


Figure 4