

3.20.2 Electricity Paper 2 (448/2)

1 STATION 1

Using the components, materials and equipment provided, carry out the following tasks:

- (a) Connect the circuit as shown in **figure 1**. Let the examiner check your work. (7 marks)

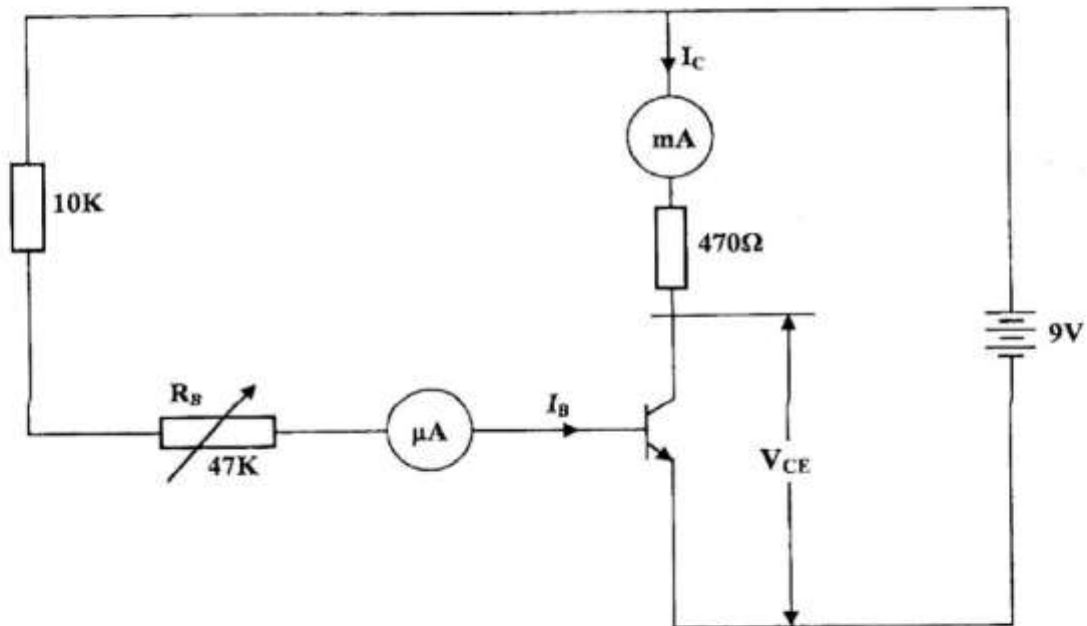


Figure 1

- (b) Vary the base resistance R_B to obtain each of the base current I_B values shown in **table 1**. For each value of I_B , measure and record in the table the corresponding values of V_{CE} and I_C . (6 marks)

Table 1

| $I_B (\mu A)$ | $V_{CE} (V)$ | $I_C (mA)$ |
|---------------|--------------|------------|
| 200 | | |
| 220 | | |
| 240 | | |
| 260 | | |
| 280 | | |
| 300 | | |

- (c) Using the values in table 1:
- (i) determine the current gain β when $I_B = 240 \mu A$. (2 marks)
 - (ii) plot a graph of I_C against V_{CE} . (5 marks)

2 STATION 2

Using the tools, equipment and materials provided, fabricate the saddle bracket shown in figure 2. (20 marks)

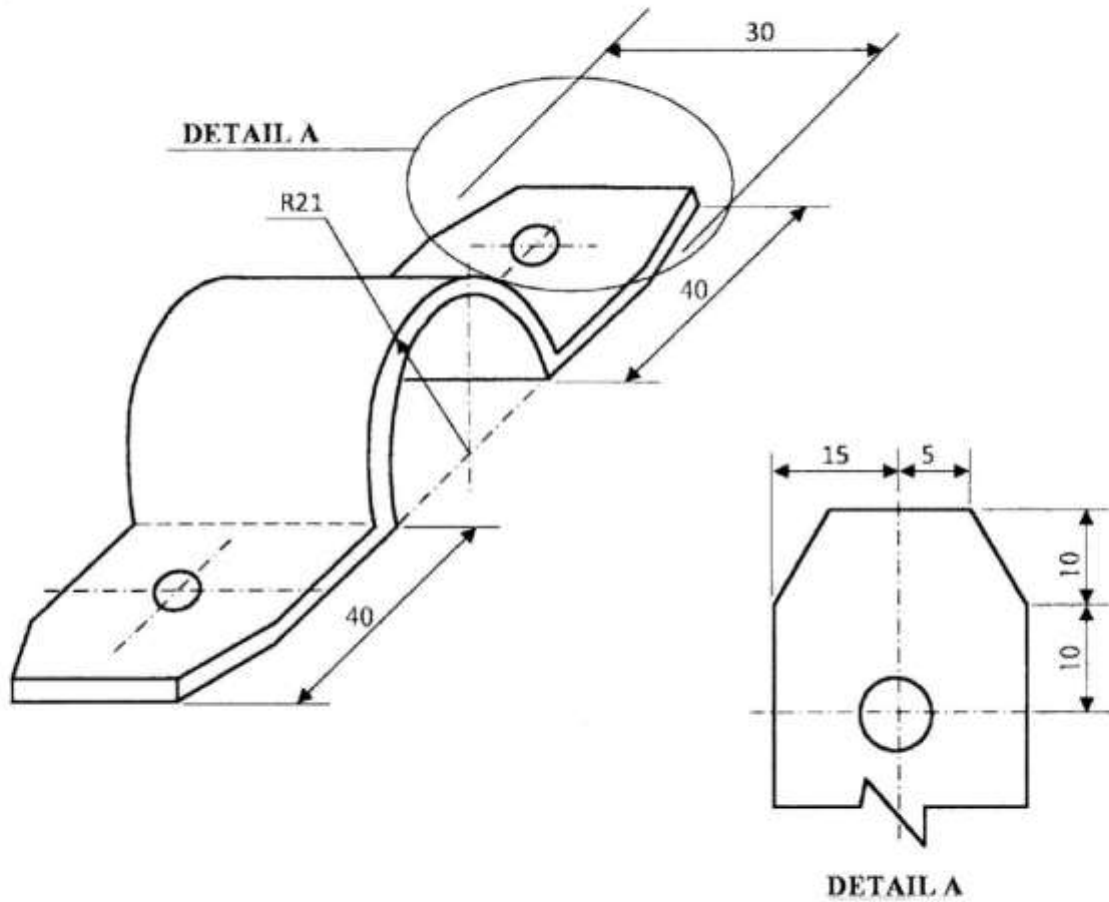


Figure 2

3 STATION 3

Using materials, components and equipment provided, perform the following tasks:

- (a) Connect the circuit shown in figure 3. Let the examiner check your work.

(5 marks)

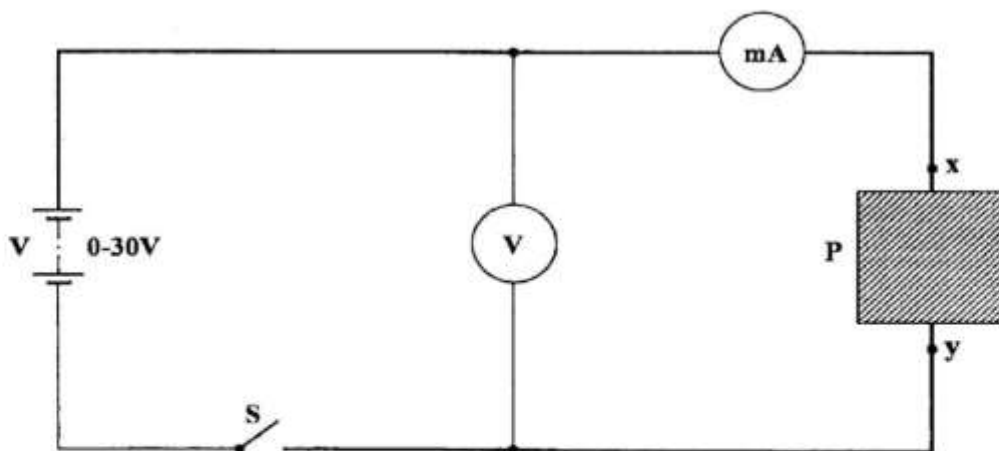


Figure 3

- (b) Close the switch S and adjust the power supply to obtain voltage values shown in **table 2**. For each voltage obtained, measure and record in the table the corresponding value of current.

Table 2

| | | | | | | |
|------------------------|-----|-----|-----|------|------|------|
| Voltage, V (V) | 2.0 | 5.0 | 8.0 | 12.0 | 16.0 | 22.0 |
| Current, I (mA) | | | | | | |

(6 marks)

- (c) Using the values in **table 2**, draw the graph of current I against voltage V. (5 marks)
- (d) Determine the slope of the graph. (3 marks)
- (e) Name the electrical quantity expressed by the slope of the graph and name its unit. (1 mark)

4 STATION 4

Figure 4 shows the block diagram of the electronic circuit.

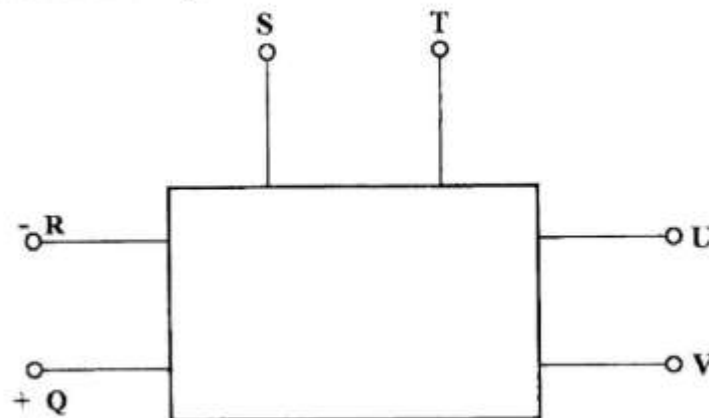


Figure 4

Use the equipment and accessories provided to perform the following tasks.

- (a) With the power supply off and output knob at minimum, connect the equipment to the terminals on circuit P as follows:-
- Q and R, a voltmeter;
 - S and T, a voltmeter;
 - U and V, a milliammeter;
 - Q and R, power supply.

(Let the examiner check your work)

(4 marks)

- (b) Turn the power supply ON. Adjust the power supply voltage to obtain the voltage values, E_s shown in **Table 3**.

In each case, measure and record in table 3 the corresponding values of Load Voltage V_L and load current I_L .

Table 3

| ES | V_{LOAD} | I_{LOAD} |
|----|------------|------------|
| 1 | | |
| 3 | | |
| 6 | | |
| 7 | | |
| 10 | | |
| 12 | | |

(9 marks)

(c) Plot a graph of load voltage V_L against power source voltage E_s . (5 marks)

(d) State **one** application of the circuit P and give the reason for your answer. (2 marks)

5 STATION 5

Using PVC sheathed wiring, complete the installation shown in **figure 5**, such that the bell is operated from either A or B. (20 marks)

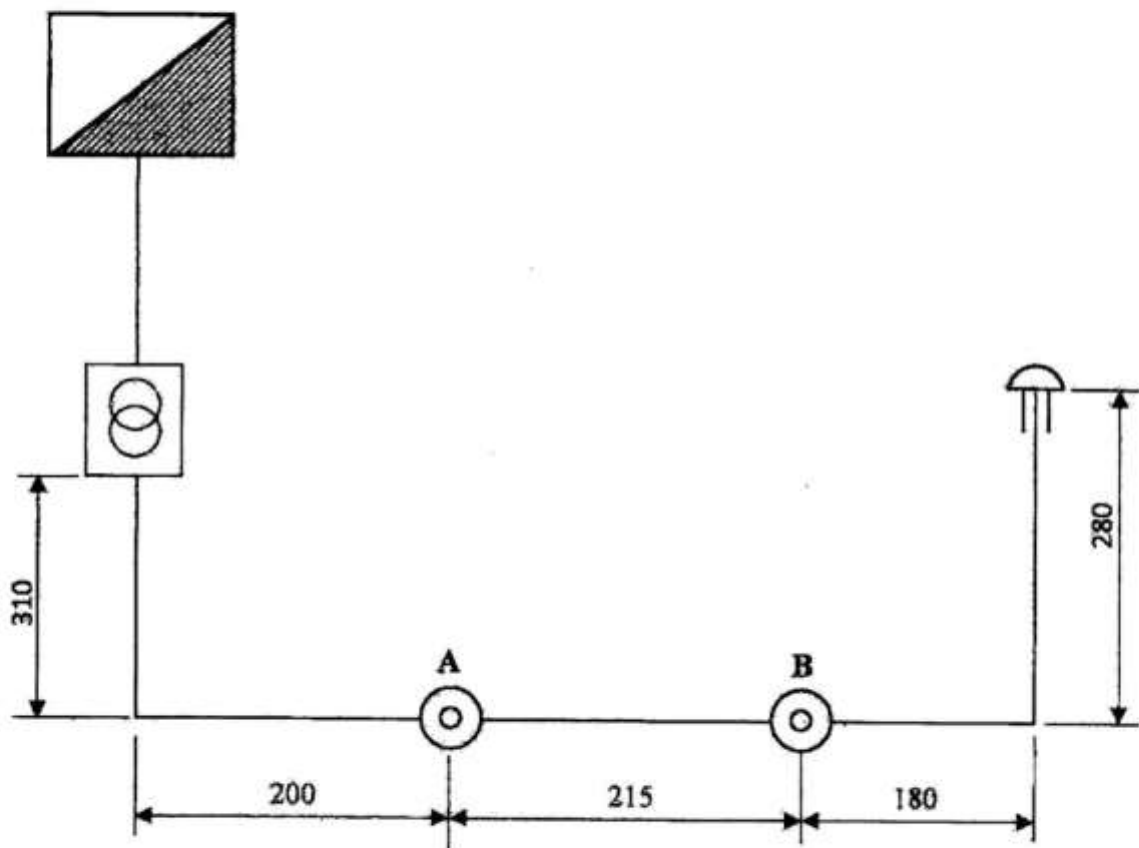


Figure 5