

Marking scheme

232/3

PHYSICS PAPER 3

(PRACTICAL)

TIME: 2 ½ hours

MOMALICHE JOINT EXAMINATION

Kenya Certificate of Secondary Education

PHYSICS (PRACTICAL) Paper 3

TIME: 2 ½ HOURS

Instructions

- Write your name, index number and admission number in the spaces provided above.
- Sign and write the date of examination in the spaces provided above.
- Answer ALL questions in the spaces provided in the question paper.
- You are supposed to spend the first 15 minutes of the 2 ½ hrs allowed for this paper reading the whole paper carefully before commencing your work.
- Marks are given for a clear record of the observations actually made, their suitability, accuracy and the use made of them.
- Candidates are advised to record their observations as soon as they are made.
- Non-programmable silent electronic calculators and KNEC mathematical tables may be used except where stated otherwise.
- This paper consists of 8 printed pages.
- Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

For Examiner's Use Only

Question 1	c	d	g	H	i	(j)	(k)	TOTAL		
Maximum Score	1	1	8	5	2	2	1	20		
Candidate's Score										
Question 2		c	e	f	g	h	i	j	k	TOTAL
Maximum Score		1	6			5	3	3	2	20
Candidate's Score										40

Question one


GRAND TOTAL

You are provided with the following:

- 2 new dry cells size D
- A cell holder
- A switch
- A milliammeter of range 0 to 1 mA
- A capacitor labeled C
- 8 connecting wires; at least four with crocodile clips on one end
- A stopwatch
- A carbon resistor labeled **R**

Proceed as follows

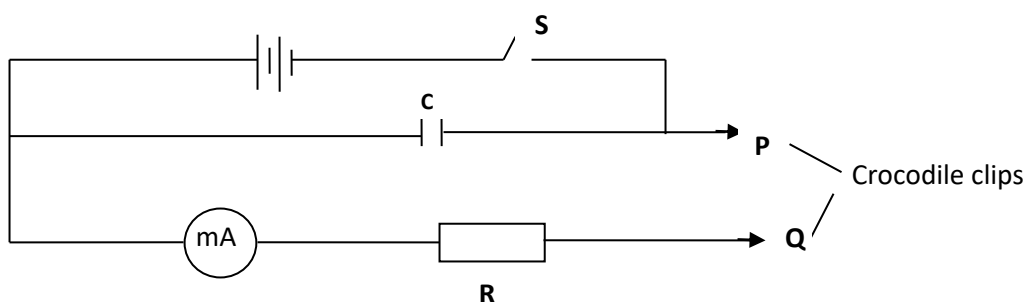- a. Connect the circuit as shown in the **figure 1** below, where **P** and **Q** are crocodile clips.



- b. Close the switch **S**
- c. Name the process which takes place when the switch **S** is closed

Charging (1 mark)


- d. Connect the crocodile clips **P** and **Q**. Observe and record the highest reading of the milliammeter **I₀** (This is the current at $t_0 = 0$)

$$I_0 = 0.61 \text{ mA} \begin{matrix} + \\ - \end{matrix} 0.02 \text{ (1 mark)}$$

- e. While the milliammeter show the maximum value of current I_0 , open the switch S and start the stop watch simultaneously. Stop the stop watch when the current has dropped from I_0 to 0.5 mA. Read and record in the table below the time taken
- f. Reset the stop watch and close the switch. Repeat the procedure in (e) to measure and record the time taken for the current to drop from I_0 to each of the other values shown in the table below. (8 marks)

Current I (mA)	0.5	0.4	0.3	0.2	0.1
Time t (s)	0.20	0.26	3.7	6.50	8.6

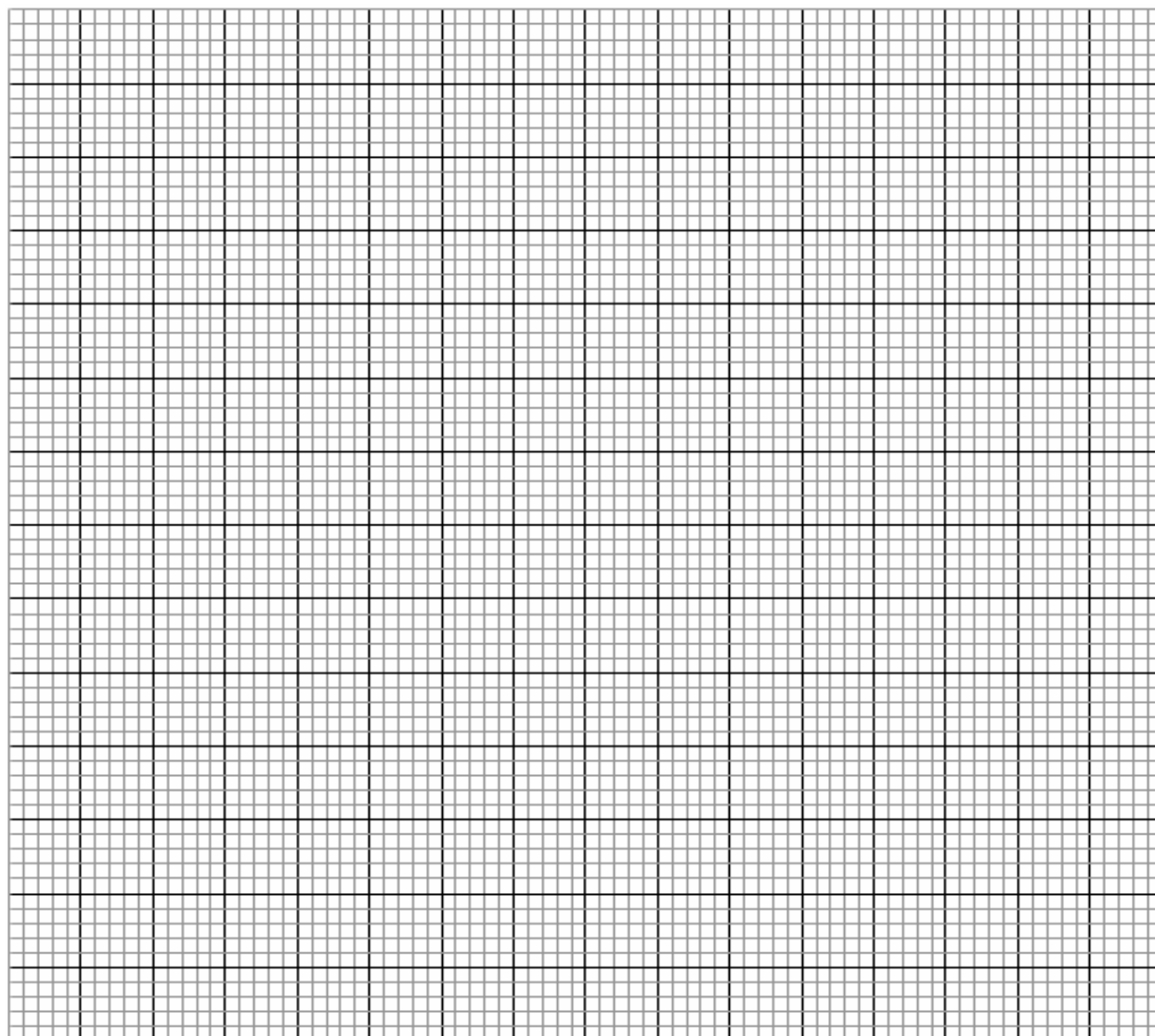- g. Plot a graph of Current I (y – axis)(mA) against time t (s) (5 marks)



- h. From your graph, find **W** the value of **I** when **t = 10s**. (3 marks)

$$W = 0.23$$

(confirm the value from graph)

- i. Given that **A = 10W**, determine the value of **A**. (3 marks)

$$A = 10 \times 0.23 \times 10^{-3}$$

- j. Determine the voltage across **R** at **t = 10s** given that $R = 4.7\text{k}\Omega$ (2 marks)

$$V = IR$$

$$= 2.3 \times 10^{-4} \times 4.7 \times 10^3$$


Question Two

You are provided with the following;

- a rectangular glass block
- 4 optical pins
- 2 thumb pins
- a soft board
- a plain paper

Proceed as follows:

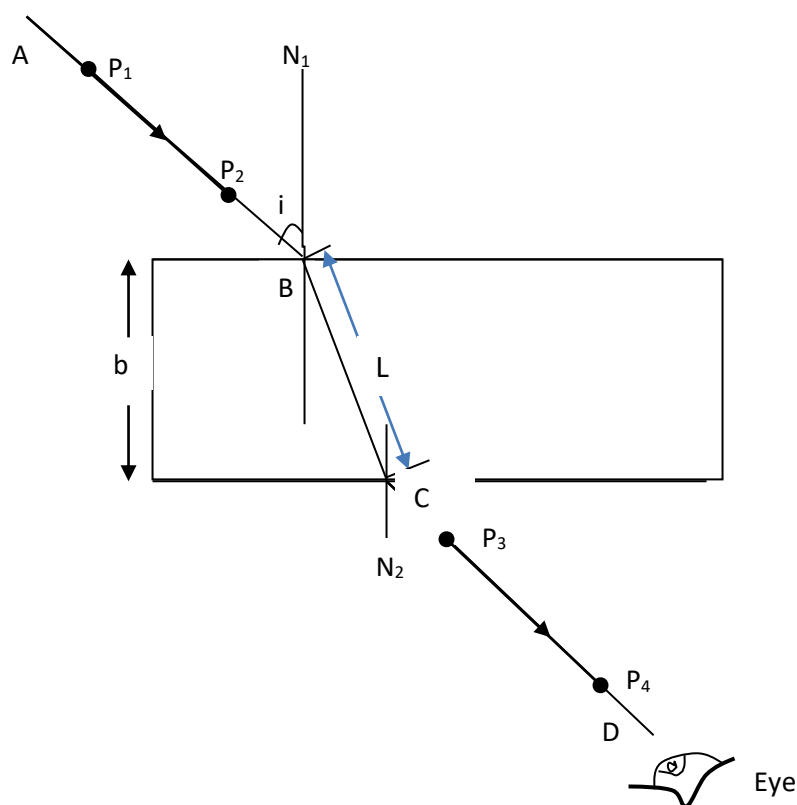- (a) Place the glass block on the plain paper with one of the largest face upper most. Trace round the glass block using a pencil as shown below.



- (b) Remove the glass block and construct a normal at B. Construct an incident ray AB of angle of incidence, $i = 20^\circ$.

- (c) Measure the breadth **b** of the glass block

$$\text{breadth } \mathbf{b} = 6.0 \begin{matrix} + \\ - \end{matrix} 0.2 \quad (1 \text{ mark})$$

- (c) Replace the glass block and trace the ray ABCD using the optical pins.
- (d) Remove the glass block and draw the path of the ray ABCD using a pencil.
- (e) Measure the length L and record it in the table below


Angle i°	L (cm)	$L^2 \text{ (cm)}^2$	$\frac{1}{L^2} \text{ (cm}^{-2}\text{)}$	$\text{Sin}^2 i$
20	6.2			0.1170
30	6.4			0.25
40	6.7			0.4312
50	7.1			0.5868
60	7.4			0.75
70	7.6			0.8830

(6 marks)

- (f) Repeat the procedure above for the angles of incidence given.
- (g) Calculate the values of $\frac{1}{L^2}$ and record in the table above.

(h) Plot a graph of $\frac{1}{L^2}$ (y-axis) against $\text{Sin}^2 i$.

(5 marks)

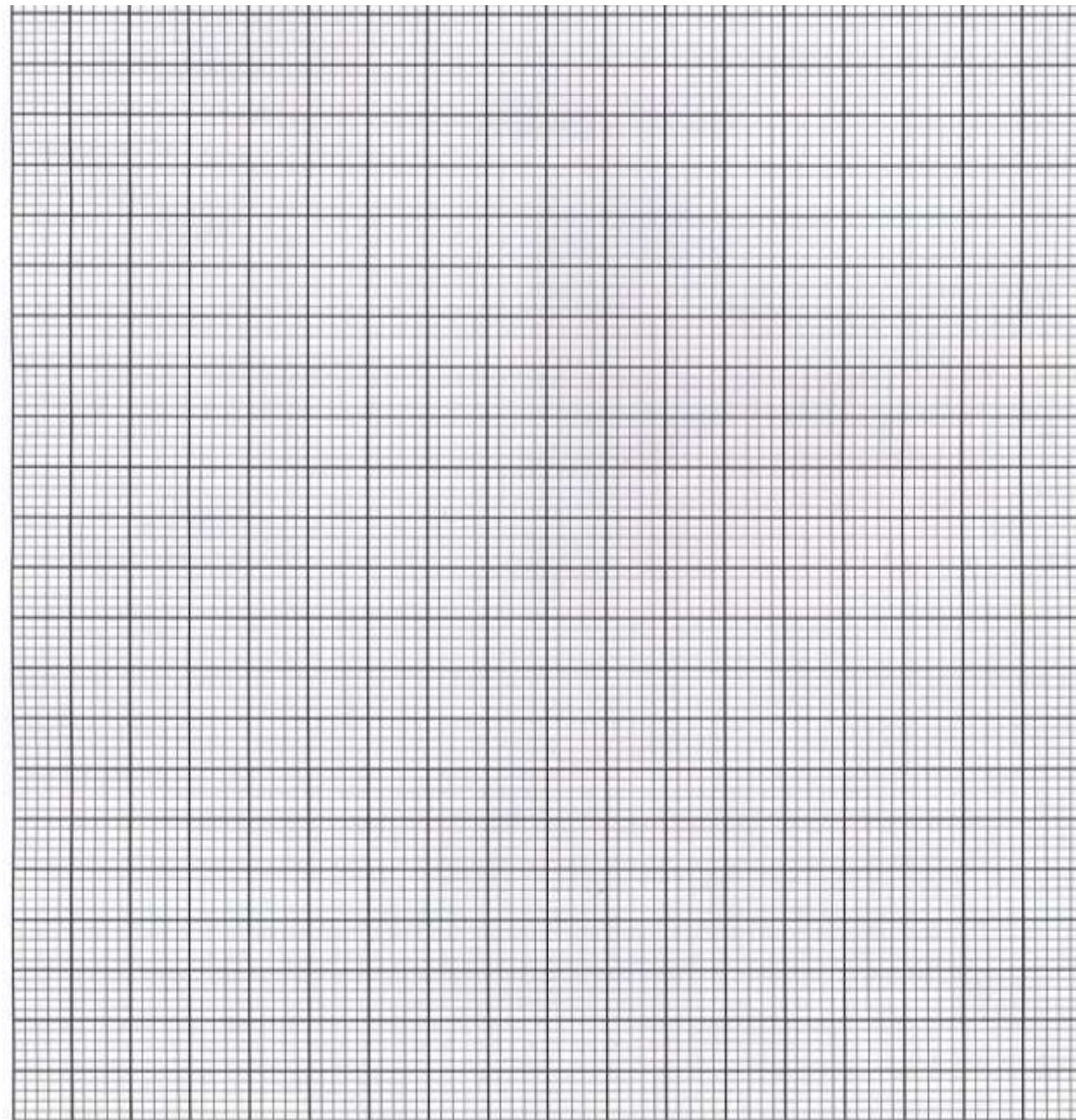

(i) Calculate the gradient **S** of the graph

(3 marks)

$$\text{Slope} = \frac{\Delta \frac{1}{2}}{\Delta \sin^2} = \frac{(24-10) \times 10^{-3}}{(14-3) \times 10^{-1}} = \frac{0.14}{1.1}$$

$$= 0.0127272 \text{ cm}^{-2}$$

Given that the equation of that graph is; $\frac{1}{L^2} = - \left(\frac{1}{n^2 b^2} \right) \sin^2 i + \frac{1}{b^2}$

(j) Determine the value of n (3 marks)

$$\text{Gradient} = 0.017272 = \frac{1}{n^2 b^2}$$

$$\frac{1}{n^2} = 0.4581812$$

$$n = 1.47734$$

(k) Present your work sheet; attached to the exam paper (2 mark)

Confirm that the student

Presents a correct worked out diagram